

"Short circuit
current"

① 9V out setting

Input V	Output I
9.96	3.47
8.99	3.17
12.16	3.17
13.41	3.17
15.27	3.17
15.27	5.30
11.16	3.21

In V 18V Set V 9V went out at ~ 5-6A

In V 22.4V Set V 18V out ~~12~~ 6A b/f screen
Shut off

CC CV Converter Validation w/o battery

	Input V	Input I	Output V	Output I
No load	12V	0A	1.2V	0A
CV	12V	0	11.8	0
	12V	0	5.04	0
	11V		5.04	
Voltage	10V		5.04	
MM	9.1V		5.04	
	7.95V		5V.04	
	7.		5.04	
	6V		5.04	
	13.1		5.08	
	14.2		5.08	
	15.12		5.06	
	15.12		6.05	
	15.12		14.98	
	11.16	0A	7.02	0A
No load	11.16	0.14	0.45	40% 1.07
CC	11.16	0.95 0.34	0.95	2.03/2.14
Current				2.84A/
MM				(a) 2.84A max (7)
@ 9V	11.16	0.02A	9.05	0.
				2.84A again
	11.16	0.56	1.35	3.02
	11.16		0.55	3.04/3.21
	11.16		0.80	4.16 max @ 9V

Bring everything to ground first
Full Saturation, Tor gates high voltage

H-Bridge Validation

Truth table

	EN	1A	2A	Function
①	H	L	H	"Right"
②	H	H	L	"Left"
③	H	L	L	"Stop"
④	L	X	X	"Stop"

0V power supply

Function	Output
1	-0.554 mV
2	11.39 V / 11.46 V
3	11.46 V
4	-6.4 mV

When switching will "overload" (PS) is cause amperage to drop to ~0.5A, is this a problem w/ just power supply?

12.04 V power supply w/ H-bridge gates 3 3/4

EN	4A	3A	Function
H	L	H	-11.46 V "Left"
H	H	L	11.46 V "Right"
H	L	L	0.07 mV "Stop"
L	X	X	-6.6 mV "Stop"



12.04V P.S. w/ 9V converter (CV) w/ H-bridge 3/4

EN	4A	3A	Function
H	L	H	-8.5 V
H	H	L	8.5 V
H	L	L	0.08 mV
L	X	X	-6.2 mV

12.04 P.S. w/ 1A conv(w/ H-bridge 3/4

EN	4A	3A	Func
H	L	H	-1.06A
H	H	L	1.03A
H	L	L	0.0007mA
L	X	X	0.0001mA

$$0.25 \text{ W} = (9 \text{ V}) \times I$$

$$V = IR$$

$$\frac{9}{0.33} = R$$

$$R = 27 \Omega$$

$$30 \Omega$$

$$9 \text{ V}$$

$$I = 0.3 \text{ A} \quad P = 2.7 \text{ W}$$

$$7 \text{ V}$$

$$I = 0.23 \text{ A} \quad P = 1.63 \text{ W}$$

CH1 (yellow - battery)

CH2 (converter output - blue)

CH3 (4A input - pink)

CH4 (H-bridge output - green)

- * No switching problems (w/ voltage)
- * High power rating resistor - used to limit current through LED
- * Can force current $\frac{1}{3}$ Pass power rating of resistors

$$200 \Omega$$

$$I = 45 \text{ mA} \quad P = 0.4 \text{ W}$$

$$I = 35 \text{ mA} \quad P = 0.25 \text{ W}$$

1st - 4A \uparrow


+ out

2nd - 4A \downarrow

- out

3rd - 4A \uparrow

No output

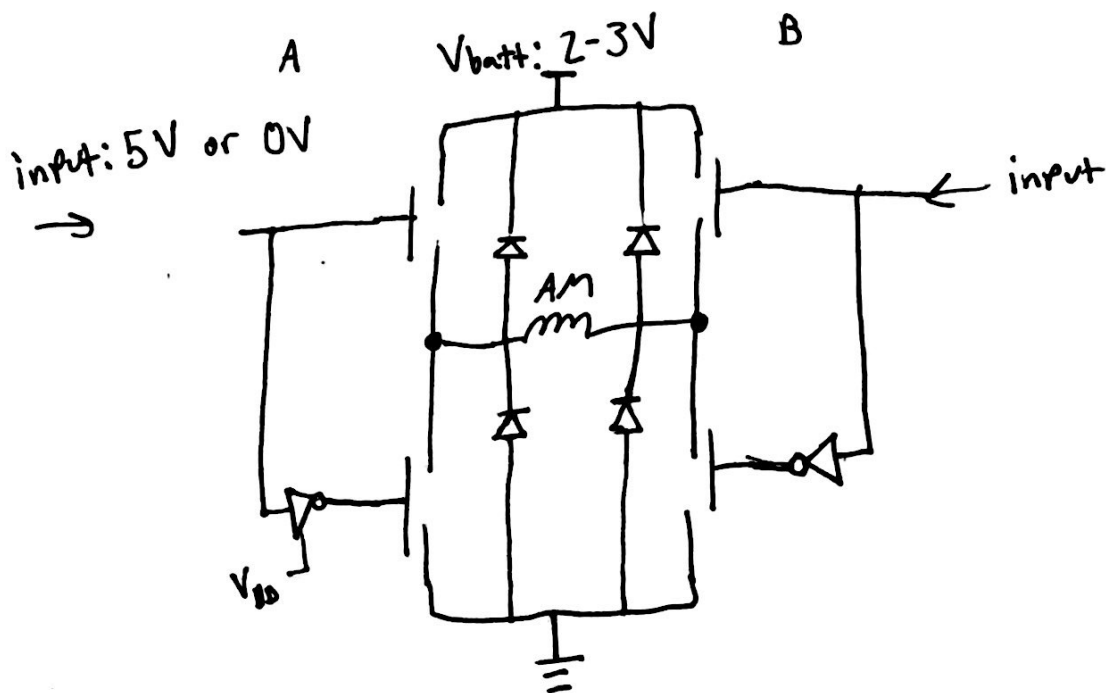


<u>A</u>	<u>B</u>	<u>Function</u>
H	L	+
L	H	-
L	L	none

Vishay IRF510PBF $V_{GS(th)} = 2V$, $I_d = 5.6A$

TI CD4069UB inverter \rightarrow TI CD4019B

74AUP1G885DC

Input			Output	
<u>PWM/EN</u>	<u>DIR</u>	<u>Z</u>	<u>BA</u>	<u>AB</u>
H	H	L	L	H
H	L	L	H	L
L	H	L	L	L
L	L	L	L	L

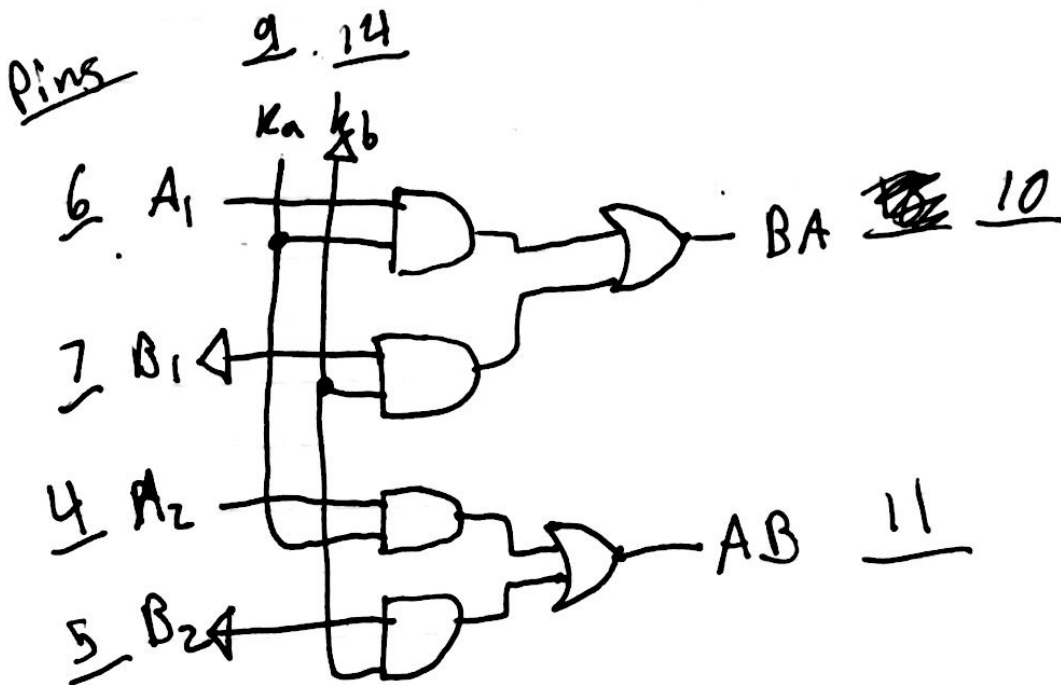

<u>K_b</u>	<u>K_a/EN</u>	<u>4A/A₁</u>	<u>3A/A₂</u>	<u>B₁, B₂</u>	<u>BA</u>	<u>AB</u>
L	H	H	H	L	H	H
L	H	H	L	L	H	L
L	H	L	H	L	L	H
L	H	L	L	L	L	L
L	L	X	X	L	L	L

Oscilloscope debugging

SS2 → video

base mode - pulling

CH1 - 3A

25ms range


CH2 - 4A

5-6V range, vibration starts, ~ 5.2V


H-bridge debug

(G) Logic V_{in} → voltage output V_{out}

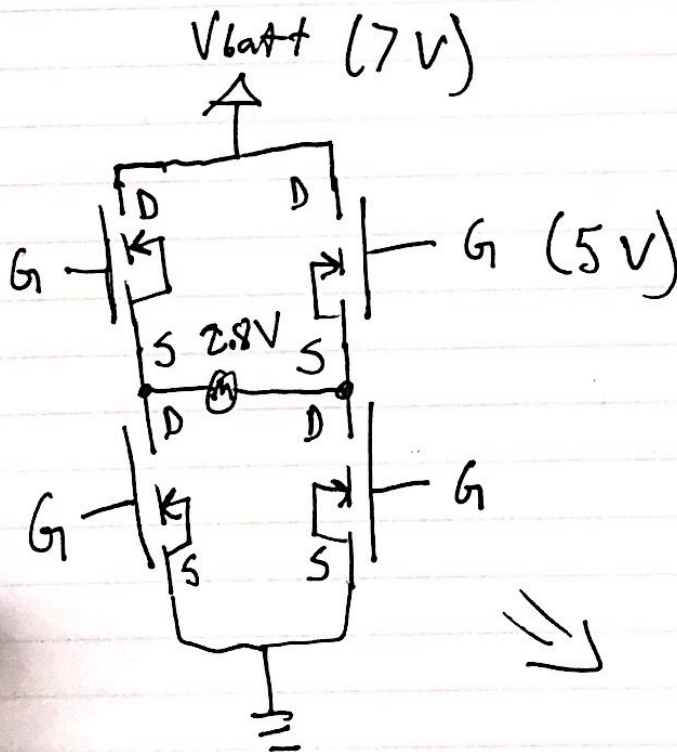(D) batt V_{in} → max 2.8V @ 5V logic / batt ≤ 2.8 , output decrea



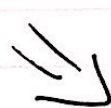Switching
orientation of
D & S → overlap
power supply



Switch

$$V_{batt} = (5V) \cdot \frac{1}{2} = 3V$$

$$G_1 = 8V \quad \frac{1}{2} = 5V$$

$$\text{then } V_m = 5V \cdot \frac{1}{2} = 2.6V$$

2.2 Ω AM in series
 separate: ^(Vixen) B = 1.08 Ω

^(Prancer) A = 1.16



Prancer

Current (A)	Force (N)
1	5
2	6
	7
	9
3	10
	10
	11
	11
4	11
	12
	15
5	14
	18
	18
	20

Vixen

Current (A)	Force (N)
1	5
1	5
1	5
2	5
	5
3	5
	8
	10
4	11
	11
	15
	15
5	15
	15
	15
	18
	20

H-bridge (high current) V_z debug

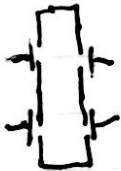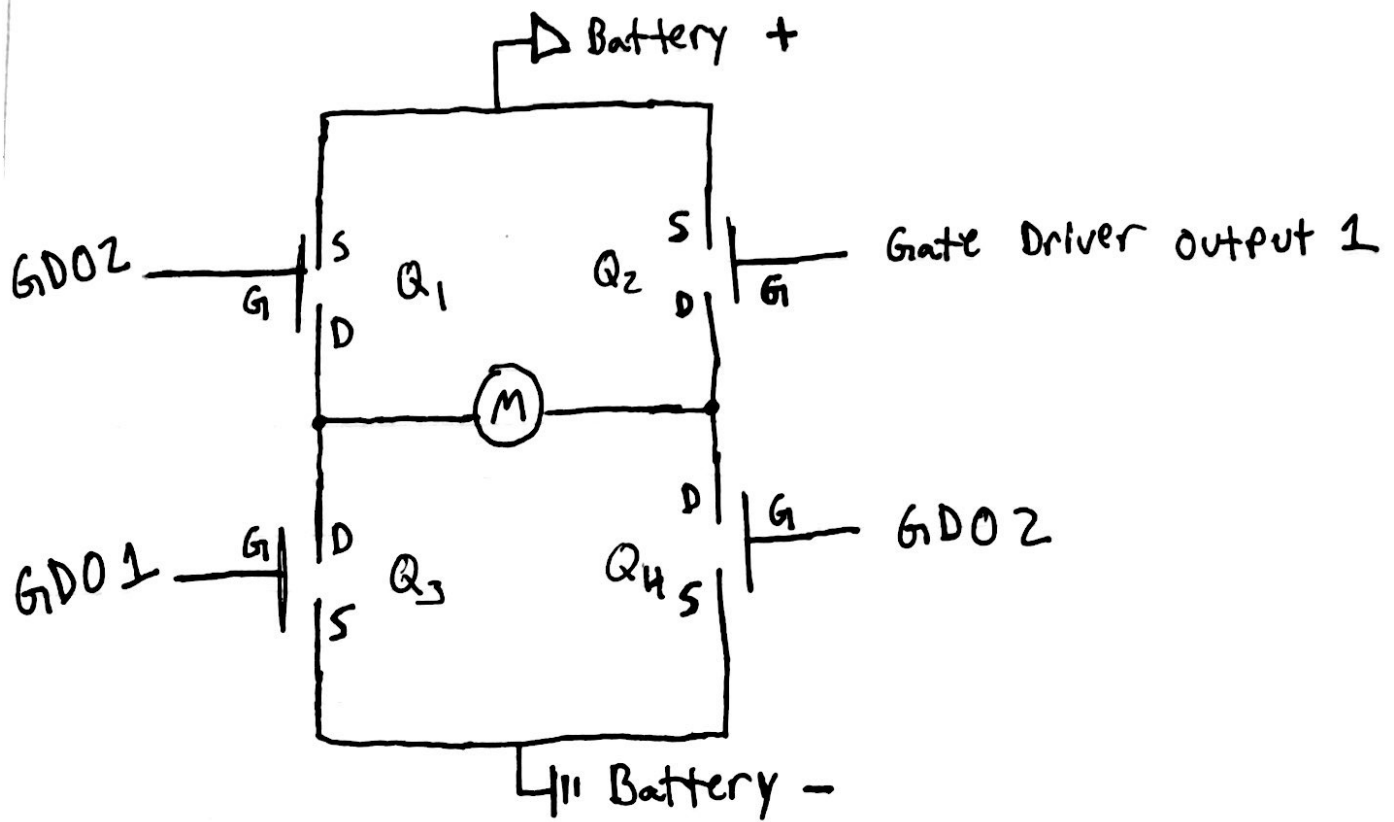

If P ^{on} ~~off~~ when (+)

If P on when (-)

GDO1⁺ GDO2⁻

GDO1⁺ GDO2⁻

Q_1
 Q_2
 Q_3
 Q_4

only allowing 1.4V above ^{Gate Voltage} to flow